A close-up photograph of a green printed circuit board (PCB) featuring two Nexperia LFPAK56 MOSFETs. The MOSFETs are black with a white "X." logo and "LFPAK56" text. The PCB has various component labels like "Q2", "Q3", "C12", "C13", "R11", "R14", "U2", and "GN" visible. An orange diagonal graphic element is overlaid on the left side of the image.

## **MOSFET Body-Diode Behaviour Benefits of Low $Q_{rr}$ & Low VSD in switching applications**

# Introduction

- Siva Uppuluri
- Senior International Product & Marketing Manager



- Richard Daley
- Power Applications Engineer



# MOSFET body diode behaviour




## Body Diode - Introduction

A Body diode occurs in ALL MOSFETs at the junction between P-N doped silicon

- Unavoidable part of the MOSFET's structure - Essential part of mosfet behaviour
- Designers exploit the body-diode in synchronous & freewheeling applications
- Allows "inductive" load current to circulate without creating voltage spikes

Like any other diode, there are limitations & losses associated with the body diode

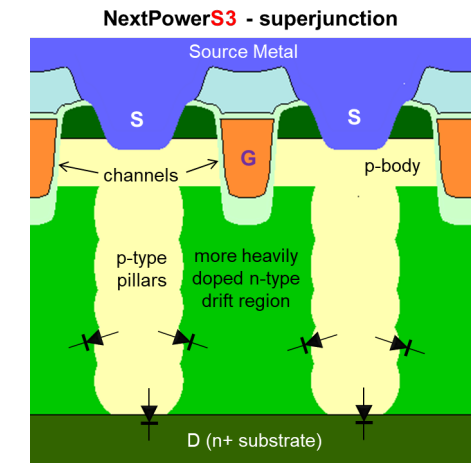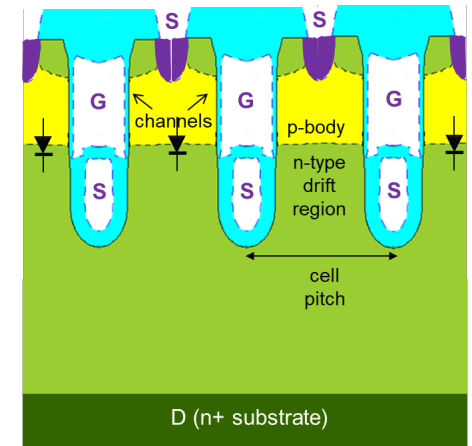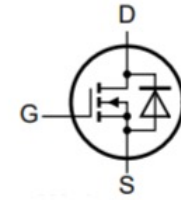- $V_F$  (or  $V_{SD}$ ) is the voltage drop across the diode (MOSFET) when it is forward biased
- $Q_{RR}$  describes the amount of stored charge, due to trapped charge carriers which accumulate around the P-N junction when the diode is forward-biased




# MOSFET body diode behaviour - $Q_{rr}$

Example: Synchronous buck / half-bridge / full-bridge

**During Dead-time** - Control FET & Sync FET are turned OFF

Body diode conducts the inductive load current

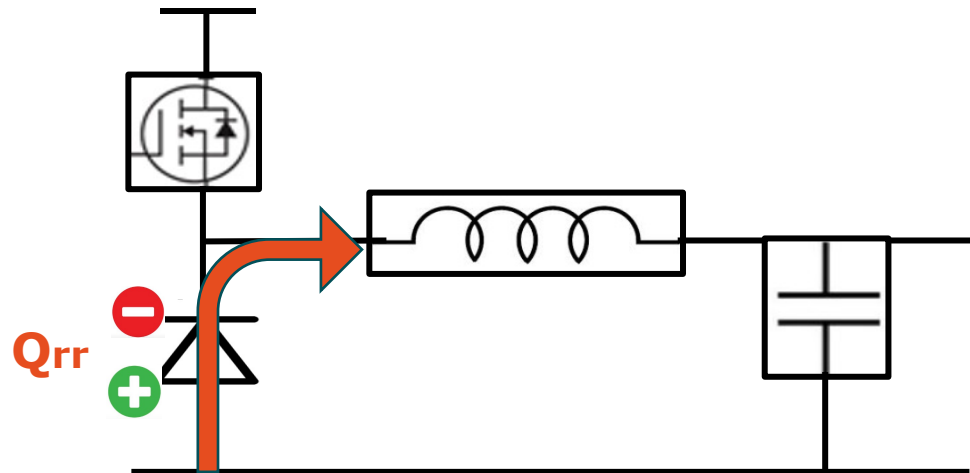Stored charge ( $Q_{rr}$ ) accumulates in the body diode



# MOSFET body diode behaviour - Qrr



Example: Synchronous buck / half-bridge / full-bridge

When the **Control FET turns ON**

Load current flows thru the high-side MOSFET + Spike current ( $I_{rr}$ ) required to deplete stored charge ( $Q_{rr}$ )

$I_{rr}$  causes additional  $I^2R$  losses in the high-side MOSFET and other components in the application

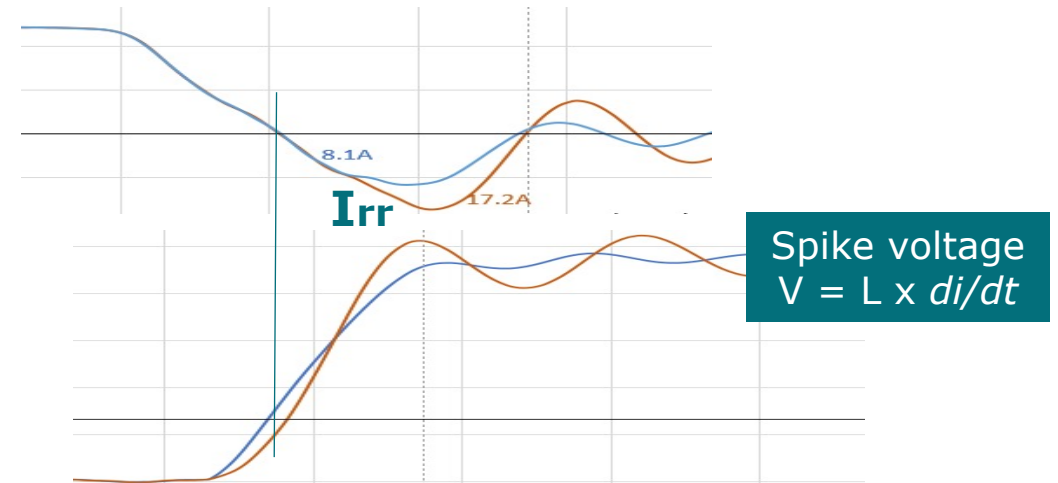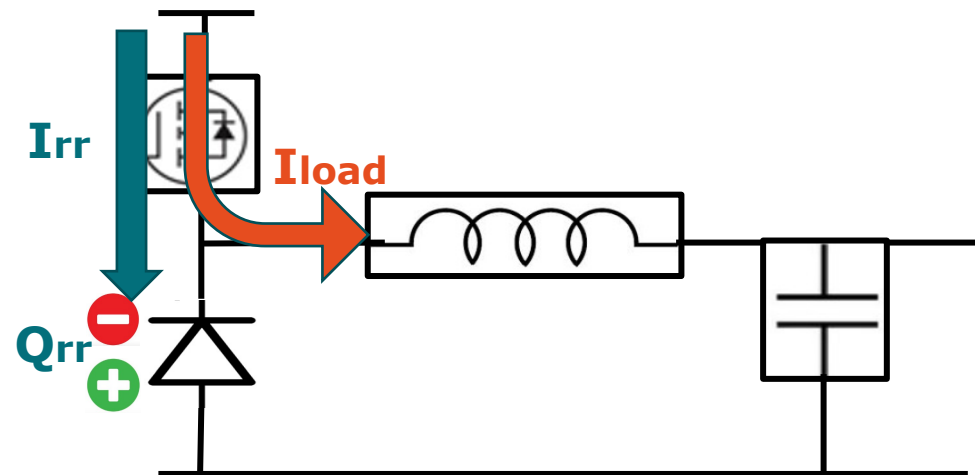$I_{rr}$  interacts with parasitic inductance in PCB & MOSFET leadframe to cause voltage spike ( $V = L \times di/dt$ )




**Low Qrr MOSFET reduces  $I^2R$  losses in the high-side MOSFET**

**Low Qrr MOSFET reduces the spike voltage**
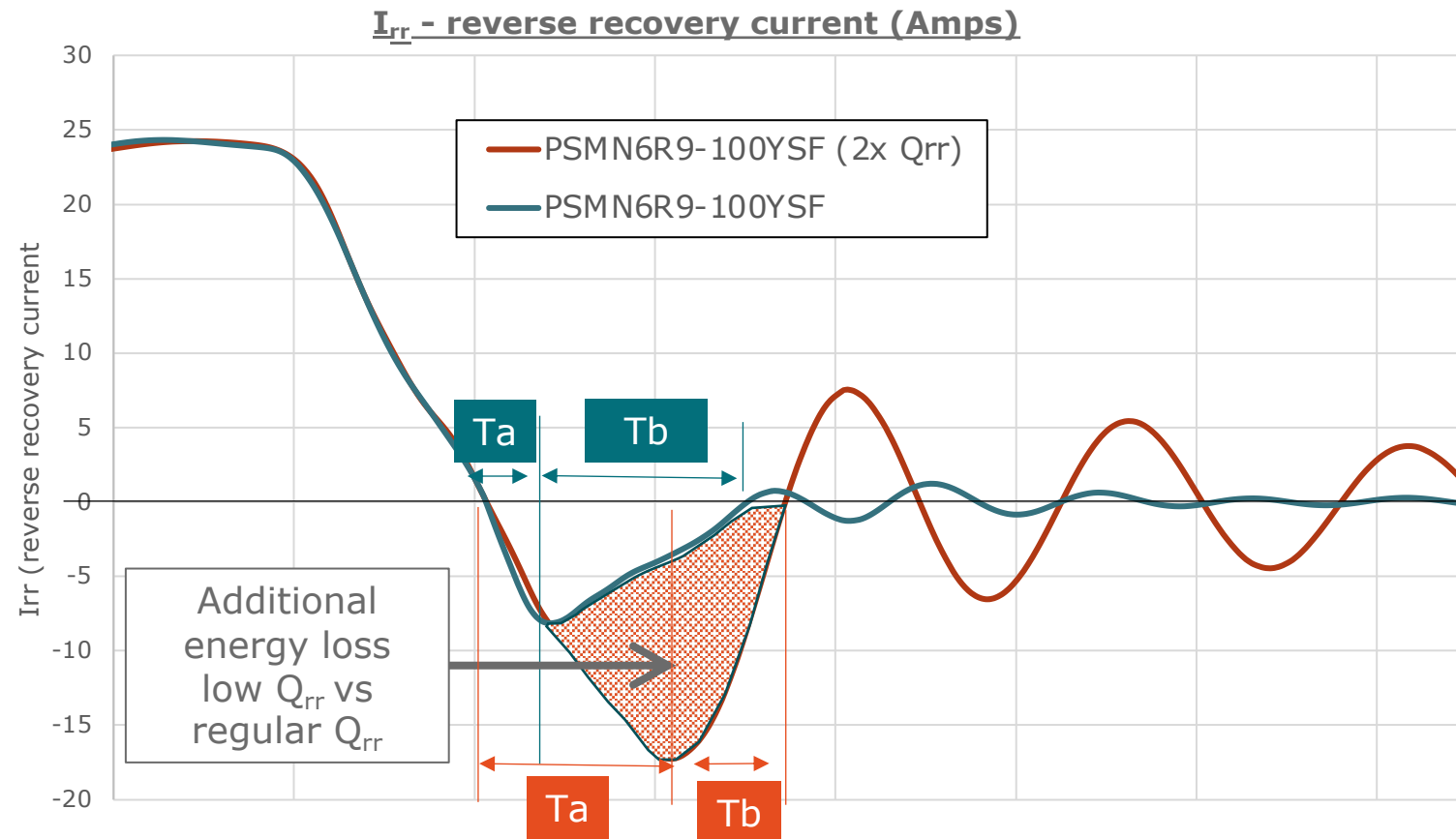
# MOSFET body diode behaviour - $Q_{rr}$

Simulating the effects of 50% lower  $Q_{rr}$




- Spice simulations show the benefits of low  $Q_{rr}$  in switching applications
- Reducing  $Q_{rr}$  by 50% gives lower current spike & lower voltage spike
- Improved softness factor ( $T_a/T_b$ ) gives reduced ringing & resonance
- Shaded area represents the additional energy loss for parts with 2x  $Q_{rr}$
- Lower  $I_{rr}$  ringing & resonance also contributes to lower EMI emissions
- Can result in shorter dead-time in some applications

**Low  $Q_{rr}$  MOSFET's + optimised damping = reduced current spiking ( $I_{rr}$ )**
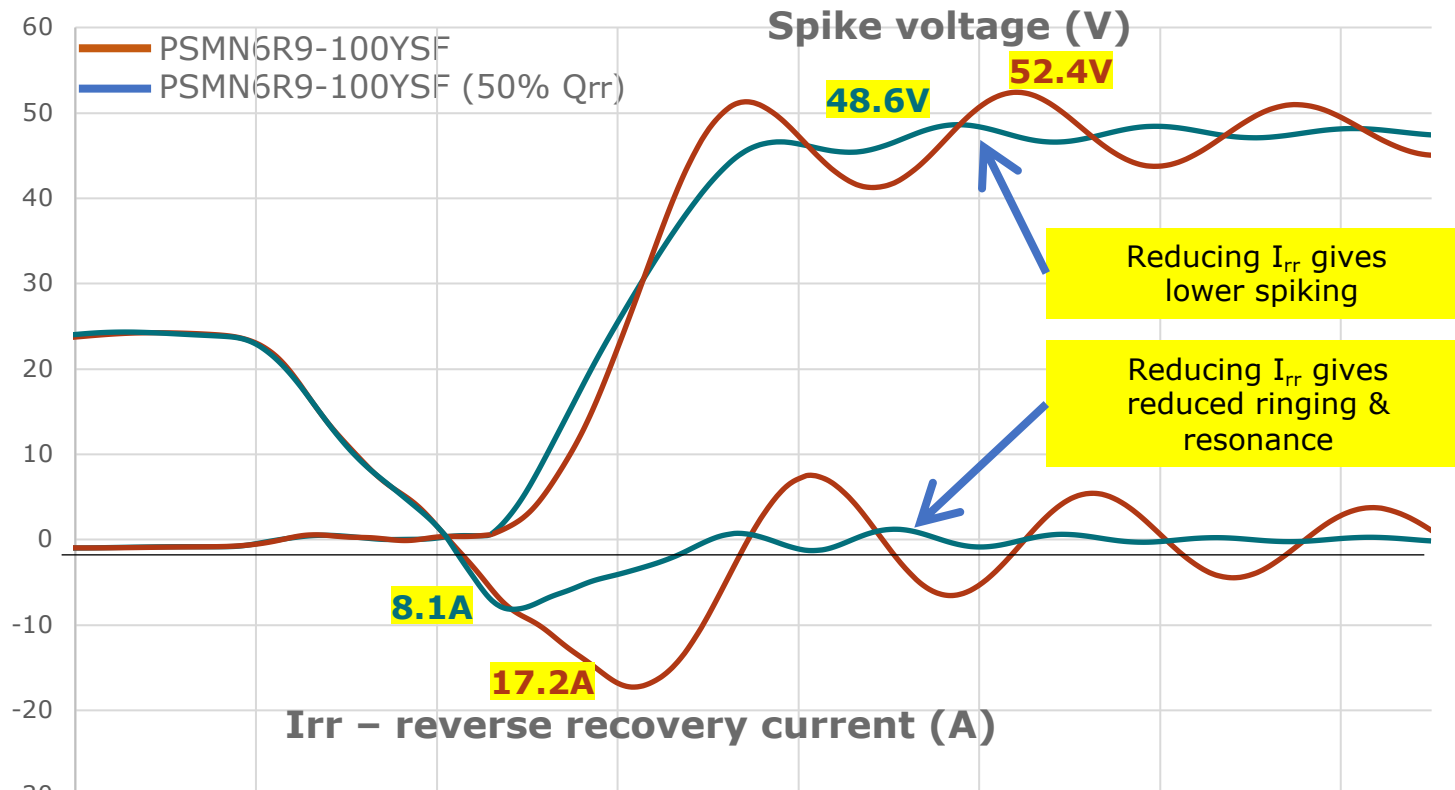
# MOSFET body diode behaviour - $Q_{rr}$

Simulating the effects of 50% lower  $Q_{rr}$



The body diode's reverse recovery current ( $I_{rr}$ ) interacts with parasitic inductance in the PCB & MOSFET leadframe resulting in a voltage spike

Lower  $I_{rr}$  current also results in lower  $I^2R$  losses in other parts of the application (eg in the high-side MOSFET)

50% lower  $Q_{rr}$  results in around 8% reduced spike voltage

$Q_{rr}$	$I_{rr}$ (Amps)	Spike Voltage (V)
100%	17.2	52.4
50%	8.1	48.6

**Reducing  $I_{rr}$  delivers reduced voltage spikes**  
**Optimised damping ( $T_a/T_b$ ) delivers lower ringing & resonance**

# MOSFET body diode behaviour – VF (VSD)

Example: Synchronous buck/ half-bridge with dead-time of 80nS

Consider an ideal mosfet with  $R_{DSon}=4m\Omega$   
conducting 20A for 80nS

$$I^2R \text{ losses} = 20^2 \times 0.004 = 1.6 \text{ Watts}$$



$$\text{MOSFET Energy loss (80nS)} = 128nJ$$

Consider a mosfet's body diode  
conducting 20A for 80nS

$$\text{Power loss} = V_f \times I(\text{load}) = 1.2 \times 20 = 24 \text{ Watts}$$

$$\text{Power loss} = V_f \times I(\text{load}) = 1.0 \times 20 = 20 \text{ Watts}$$
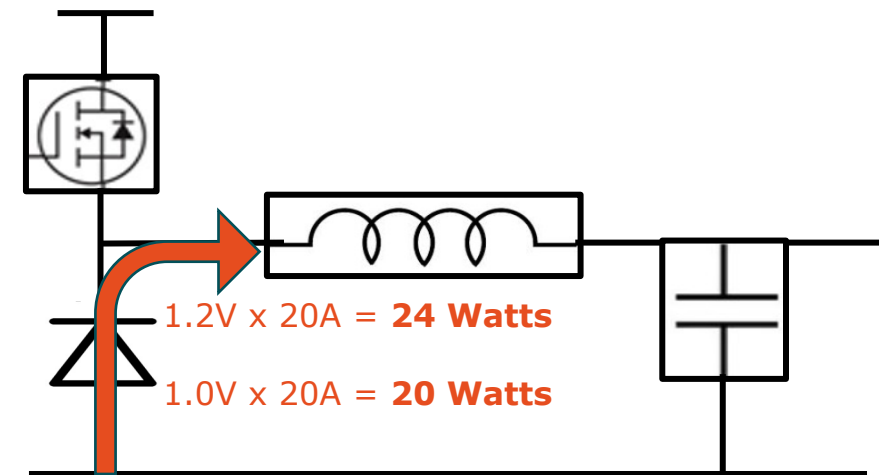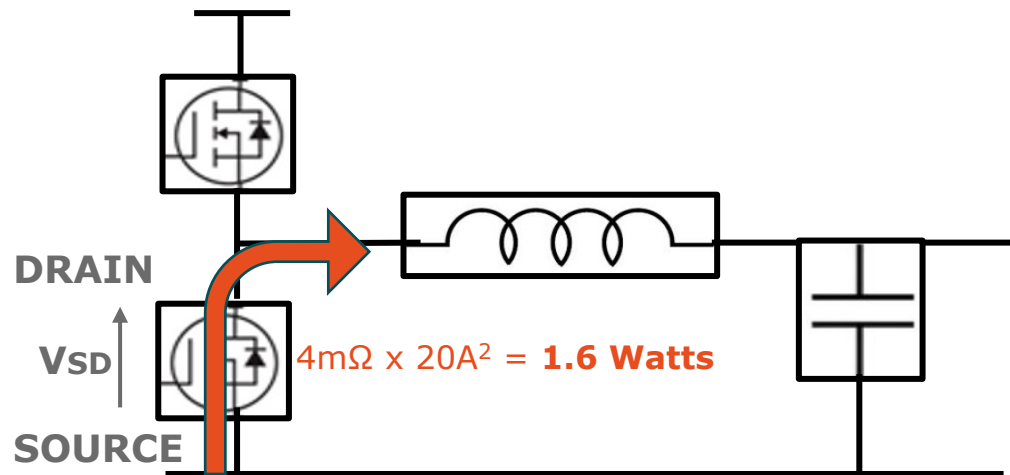
$$\text{DIODE Energy loss (80nS)} = 1920nJ$$



**Body diode losses can be x12 ~ x15 higher than when the mosfet conducts**  
**Reducing the diode's Vf results in significant efficiency gains (4 Watts)**




The background features a large, stylized white 'X' shape on the left side, set against a solid orange background. The 'X' is formed by two white, rounded rectangular shapes that intersect in the center. In the bottom right corner, there is a white semi-circle.

# **NextPower 80V/100V**

Benchmark testing

# Topology used for evaluation

Simplistic Buck Convertor – 48V to 12V

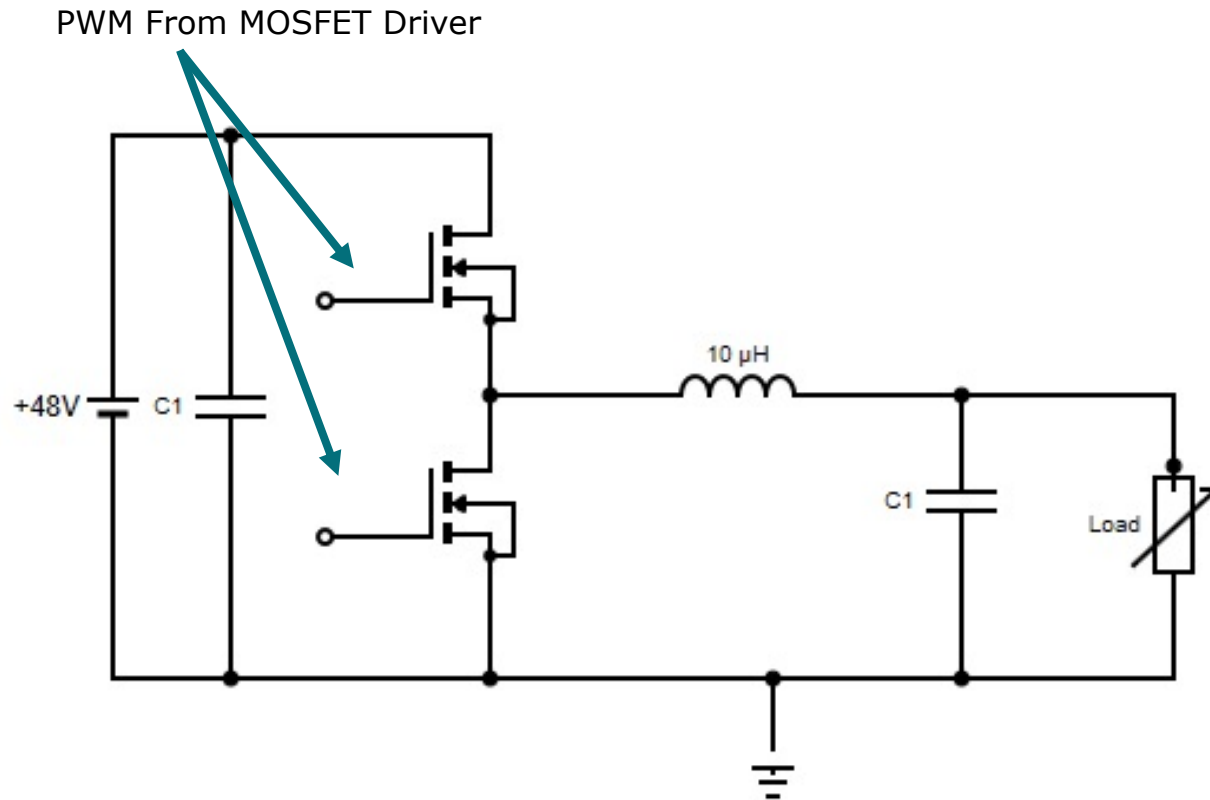

- **Simple Design – highlights MOSFET behaviour**




- Minimal additional components or tuning to give unbiased results
- Same MOSFET used in high-side & low-side
- Fixed inductor (10uH)
- Fixed gate resistor values (0 Ohms)
- Fixed deadtime across all product groups
- CCM mode (constant current)
- Sweeping load current from 2-20A

- **MOSFET Performance (100KHz-500KHz)**

- Switch-node spiking
- Efficiency vs load current
- Efficiency vs switching frequency
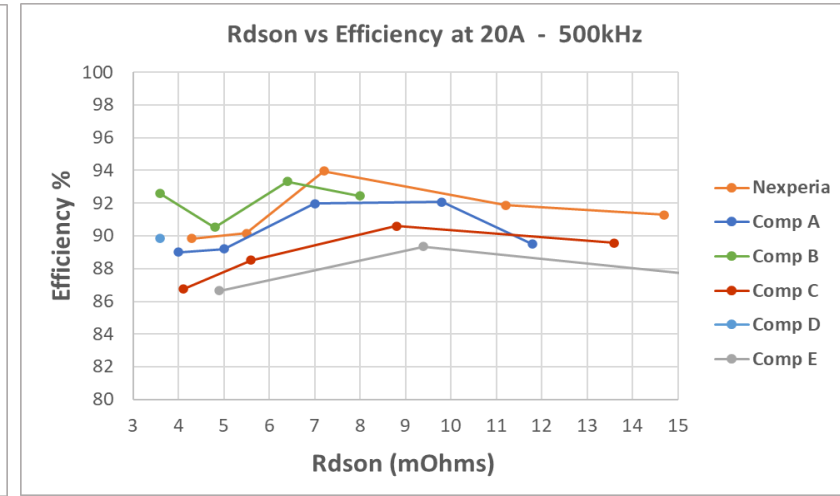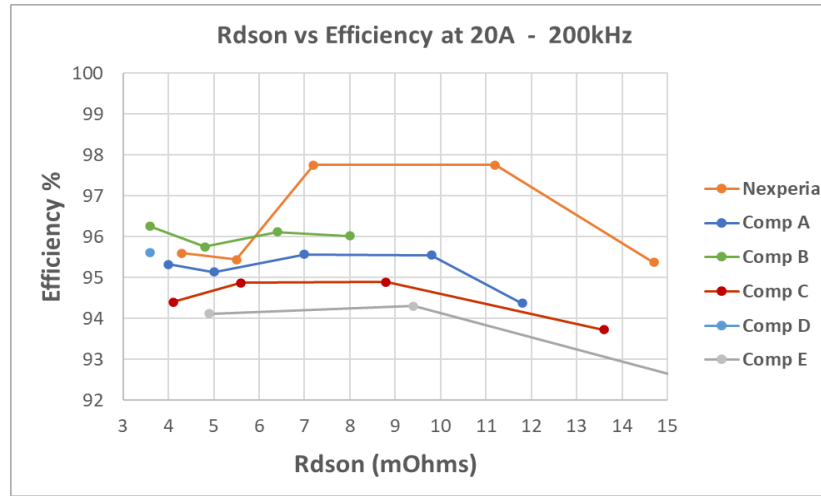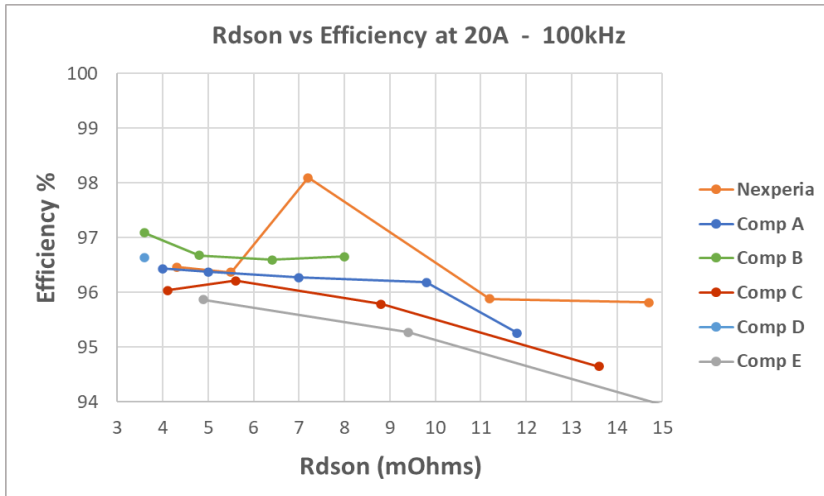
# Next Power 100V - Efficiency @20A vs competitors




Nexperia vs Leading competitor types – 100V 3mOhm to 15mOhm



Consistently strong 'efficiency @20A' from 100KHz to 500KHz  
Nexperia's 12mR~15mR are on-par with competitor 7mR~10mR
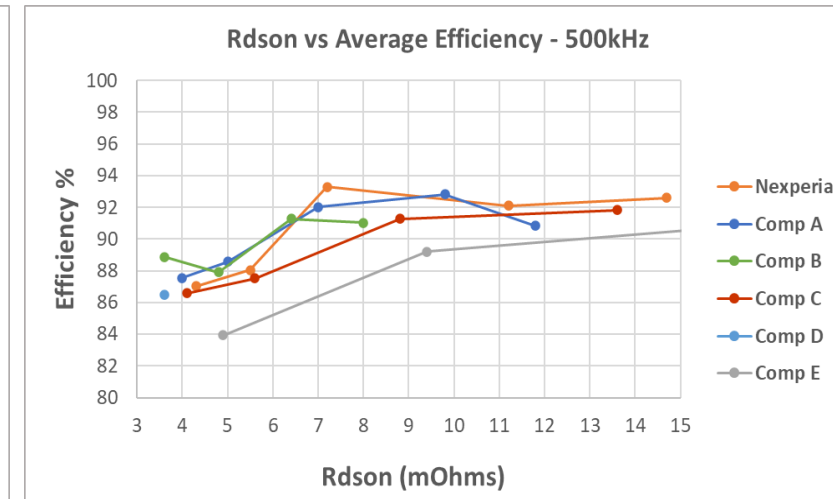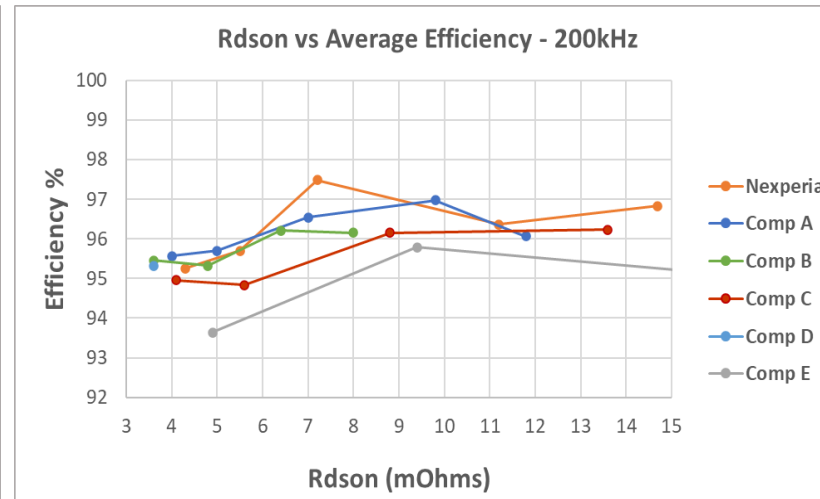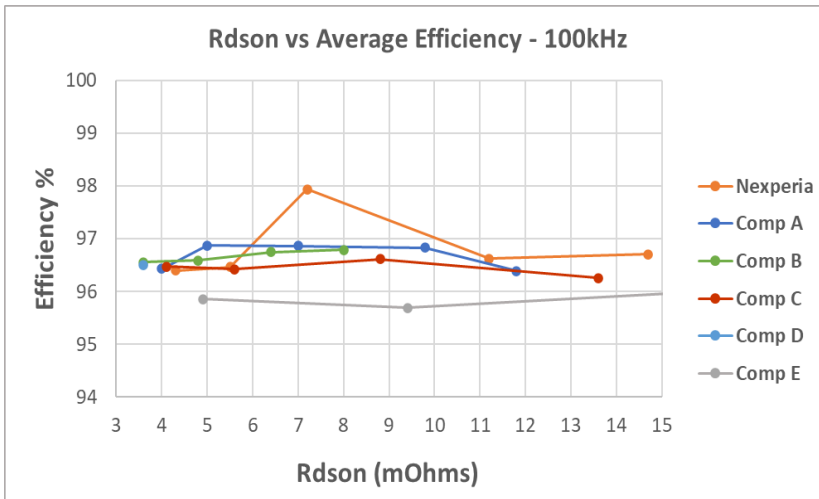
# Next Power 100V - Average Efficiency vs competitors

Nexperia vs Leading competitor types – 3mOhm to 15mOhm






Average efficiency measured at 2A,4A,10A,20A load current

Consistently strong 'average efficiency' from 100KHz to 500KHz  
Nexperia's 12mR~15mR are on-par with competitor 7mR~10mR
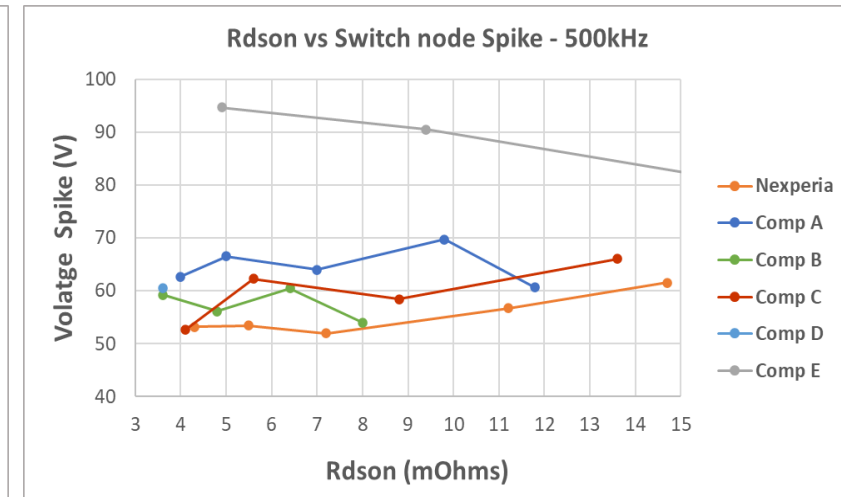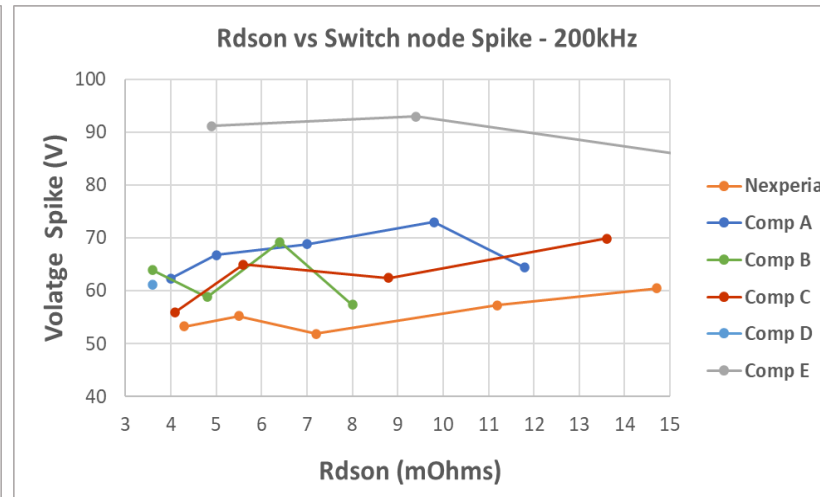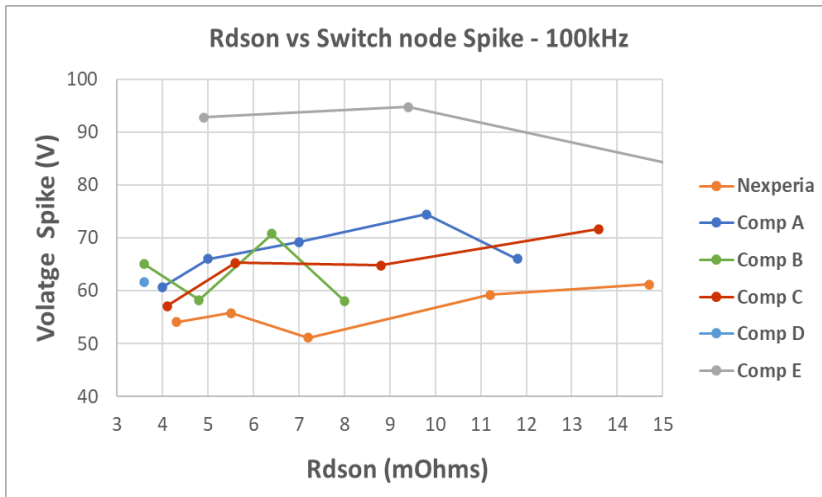
# Next Power 100V - Switch-node Spiking vs competitors

Nexperia vs Leading competitor types – 3mOhm to 15mOhm





Lowest spiking across all competitors

Spike voltage is not dependent on switching frequency

Low  $Q_{rr}$  body diode may also give reduced EMI emissions in many applications

# NextPower 80V vs NextPower 100V

NextPower 80V vs NextPower 100V

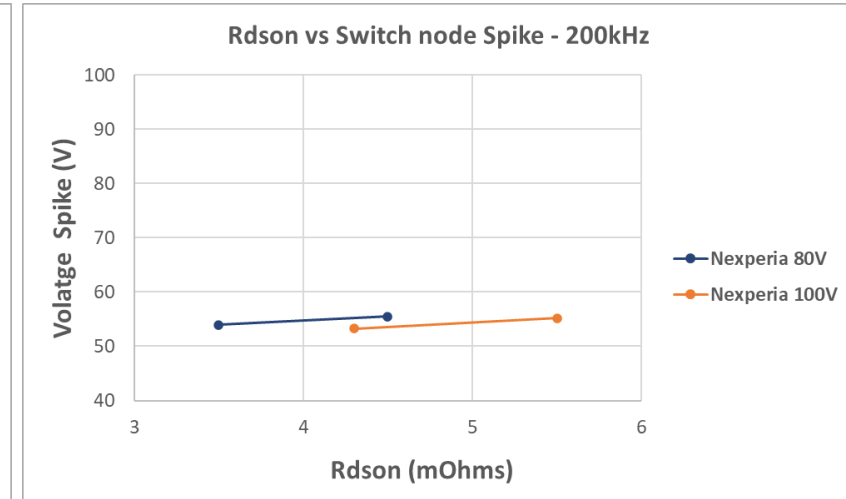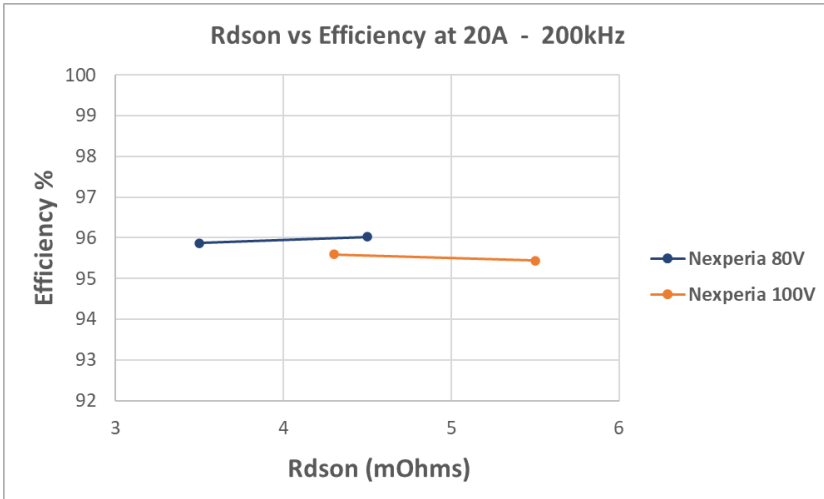


NextPower 80V – lower RDson compared to NextPower 100V

NextPower 80V - Slight efficiency improvement especially under high load

Similar low-spiking performance as NextPower 100V
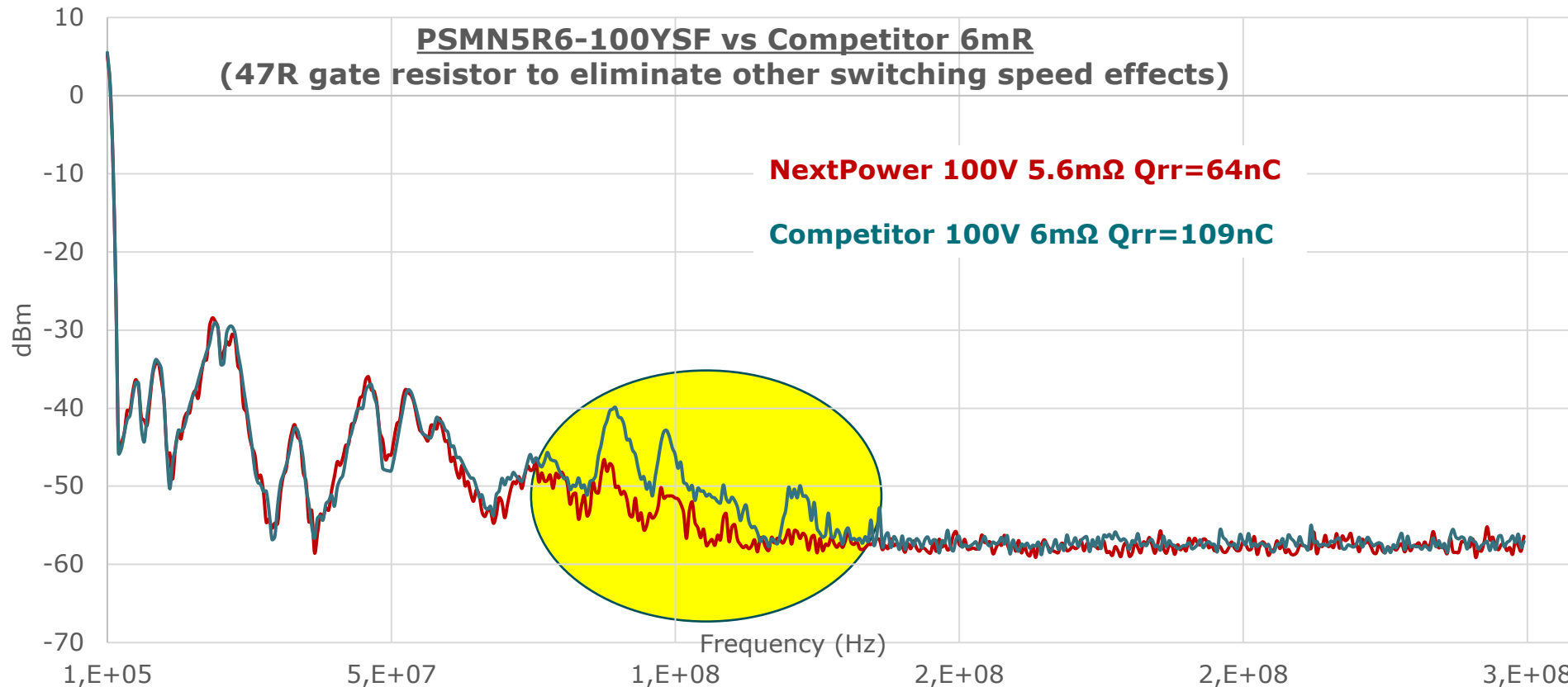
# Low $Q_{rr}$ = Lower EMI emissions

Study between high  $Q_{rr}$  (competitor) & low  $Q_{rr}$  (NextPower 100V) parts



NextPower 100V with Low  $Q_{rr}$  delivers ~10dB lower EMI emissions (80MHz ~ 150MHz)

# NextPower 80V / 100V – Technology Benefits

Low  $Q_{rr}$  & Low body-diode  $V_f$  – For high efficiency and low spiking

## Features



- Low  $R_{DS(on)}$  – 3.5m $\Omega$  @80V & 4.3m $\Omega$  @100V in LFPAK56E
- Very low  $Q_{rr}$  (60~70% lower than leading competitors)
- Optimised body-diode, low forward voltage -  $V_{SD} = 1V(max)$
- Strong avalanche rating, 100% tested at IAS > 50 Amps
- Optimised  $C_{OSS}$
- $T_j(max) = 175^\circ C$
- Wave-solderable LFPAK56 package

## Suitable for a wide range of applications

- AC/DC synchronous rectifier
- DC/DC primary & secondary side switching – 48V 4G/5G telecom applications
- BLDC Motor control (e.g. Full-bridge)
- LED lighting (e.g. flyback & boost applications)
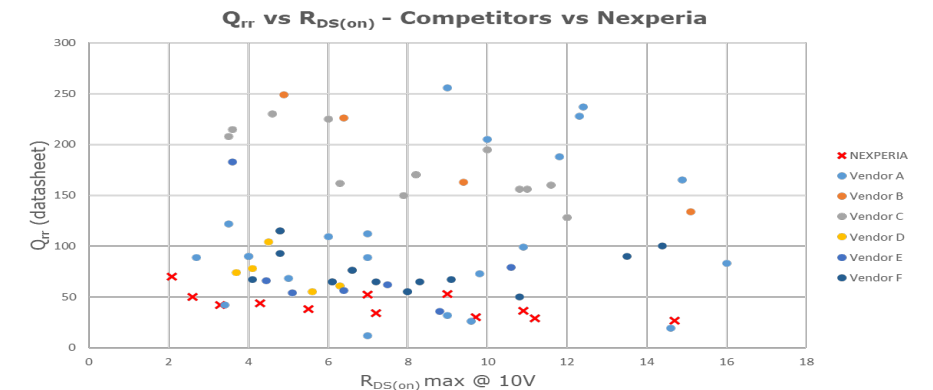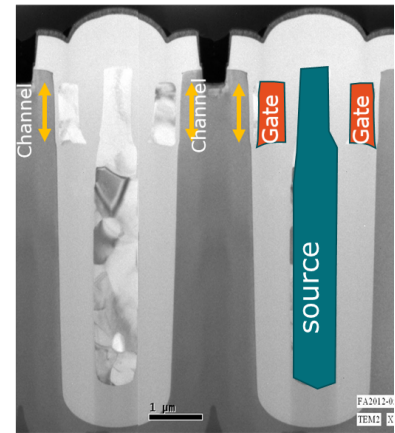
## Benefits

- Low  $I^2R$  losses & high  $I_D(max)$  rating
- Efficiency gains, low-spiking & low-ringing & EMI
- Low dead-time losses in synchronous / free-wheeling application
- Rugged & reliable switching
- Low-spiking & high-efficiency
- LFPAK types meet IPC9592 for telecom & computing applications
- Low cost manufacturing & space-constrained PCB assembly





# Design-in resources



## Request samples for Evaluation

- Speak to your local sales representative or distributor
- Buy online from the Nexperia shop - <https://www.nexperia.com/shop.html>

## Interactive Parametric search tool

- Choose a MOSFET by voltage, package, RDS(on)  
<https://www.nexperia.com/products/mosfets/power-mosfets/#parametrics>

## Datasheet & Application Data available.

- Visit the [Nexperia.com](https://www.nexperia.com) for more information  
<https://www.nexperia.com/products/mosfets/family/NEXTPOWER-80-100V-MOSFETS/>

## Hints and tips and guidance on MOSFET's & GAN products.

- Request a free copy of Nexperia application Handbook in digital and hardback form  
<https://efficiencywins.nexperia.com/efficient-products/mosfet-and-gan-fet-application-handbook.html>

Please share your  
questions and insights

EFFICIENCY WINS.